

### 2.6.3 Electrical circuit model of the Cell Membrane.

- Model the cell membrane as a capacitor (because it separates charges)

- the Capacitance of any insulation is

$$C_m = \frac{Q}{V}$$

where Q is charge across the capacitor, V is Voltage.

- two parallel conductor plates separated by an insulator of thinness of

$$C_m = \frac{k\epsilon_0}{d}$$

k is dielectric constant

$\epsilon_0$  is permittivity of flow space

- typical capacitance of cell membrane = 1.0uF/cm<sup>2</sup>

-see Fig 2.11

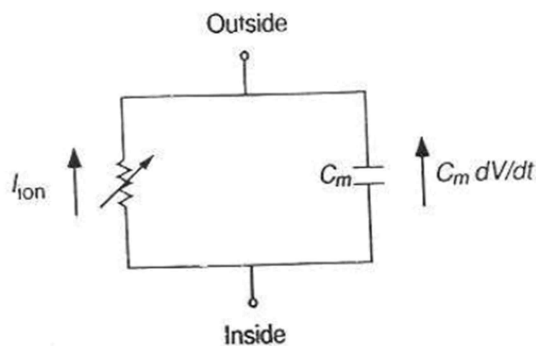


Figure 2.11 Electrical circuit model of the cell membrane.

the membrane acts like a capacitor in parallel with a resistor.

- since  $I = \frac{d\theta}{dt}$

$$C_m \frac{dv}{dt} + I_{ion} = 0$$

$$V = V_i - V_o$$

- Another common Model, consider an ion and assume the potential drop has two components by the Nernst Equation.

$$V_s = \frac{RT}{ZF} \ln \left( \frac{[s]_o}{[s]_i} \right)$$

the potential drop due to the concentration differences

- Potential drop due to an electrical current =  $rI_s$

$r$  = channel Resistance

$I_s$  = transmembrane current

$$V = rI_s + V_s$$

$$I_s = g(V - V_s) , g = \frac{1}{r} = \text{membrane conductance.}$$

Expression of  $I_{\text{ion}}$  as a linear function of the membrane potential.